國立雲林科技大學 107 學年度 碩士班招生考試試題

系所:電子系

科目:工程數學(3)

- 1. Find the solution of the equation $3x(xy-2)dx + (x^3+2y)dy = 0$. (10 %)
- 2. Find the solution of the equation $y'' 2y' 3y = 3t^2 + 4t 5$ with y(0) = 9 and y'(0) = -4. (15 %)
- 3. Find the solution of the system $\begin{cases} x_1' = 5x_1 3x_2 + 8 \\ x_2' = x_1 + x_2 + 32t \end{cases}$ with $\begin{cases} x_1(0) = 2 \\ x_2(0) = 0 \end{cases}$ (15 %)
- 4. Find the solution of the equation $y'' 3y' + 2y = 4e^{2t}$ with y(0) = -3 and y'(0) = 5. (10 分)
 - (a) Prove that the Laplace transform of $4e^{2t}$ is $\frac{4}{s-2}$.
 - (b) Solving the differential equation by using Laplace transform.
- 5. Perform the indicated operation, give that (10 分)

$$A = \begin{bmatrix} 1 & 0 & -2 \\ 2 & 2 & 3 \end{bmatrix} \quad B = \begin{bmatrix} 2 & 3 & 0 \\ 0 & -2 & 4 \end{bmatrix} \quad C = \begin{bmatrix} 1 & 2 \\ 4 & 3 \\ 0 & -1 \end{bmatrix}$$

- (a) (A+B)C (b) If 2X-6(2A-B)=0, Find X.
- 6. Find the eigenvalues and eigenvectors of A. (10 分)

$$A = \begin{bmatrix} 2 & 0 & 1 \\ 0 & 1 & 0 \\ 2 & 0 & 3 \end{bmatrix}$$

- 7. (a) A real square matrix $A=[a_{jk}]$. Define the following terms: (using by A^T , A, A^{-1})
 - (1) Symmetric matrix (2) Skew-Symmetric matrix (3) Orthogonal matrix (6 分)
 - (b) Determine the nature (Symmetric or Skew-Symmetric or Orthogonal) of the following matrices. (8 分)

$$A = \begin{bmatrix} 1 & 2 \\ 2 & 3 \end{bmatrix}, B = \begin{bmatrix} \frac{\sqrt{3}}{2} & \frac{-1}{2} \\ \frac{1}{2} & \frac{\sqrt{3}}{2} \end{bmatrix}, C = \begin{bmatrix} 0 & 9 & -12 \\ -9 & 0 & 20 \\ 12 & -20 & 0 \end{bmatrix}, D = \begin{bmatrix} 1/7 & 3/7 & 2/7 \\ 3/7 & 2/7 & 5/7 \\ 2/7 & 5/7 & 3/7 \end{bmatrix}$$

8. If $\vec{A} = 2\vec{\imath} + \vec{\jmath} - \vec{k}$, $\vec{B} = \vec{\imath} - 3\vec{\jmath} - 5\vec{k}$ Find (a) $\vec{A} \times \vec{B}$ (b) $\vec{A} \times \vec{B}$ (c) the cosθ between \vec{A} and \vec{B} (d) the projection of \vec{A} on \vec{B} . (16 $\hat{\gamma}$)


系所:電子系

科目:半導體元件

1. Explain the following terms

(a) Heterojunction	(5%
(a) Helefolunction	(5%

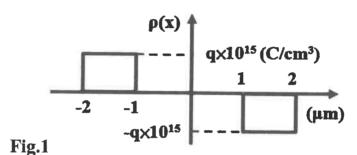2. For a pin junction, the charge distribution is shown in Fig.1. Draw the field and voltage distributions and find the applied voltage. (15%) $(n_i=10^{10}/\text{cm}^3, \text{kT}=0.025\text{eV}, \text{ln}10=2.3)$



3. Describe the reasons the dominate current is electron or hole current of (a) p⁺n and (b) p⁺N junctions, where + and N mean high doping concentration and wider band gap, respectively. (15%)

4. Explain or define the following terms:

5. Describe the advantages of direct bandgap for semiconductors. (15%)

6. Describe briefly the formation of the build-in potential in a p-n junction diode. (15%)


系所:電子系

科目:計算機概論(1)


- 1. Convert the following 2's complement binary numbers to decimal. (20%)
- (a) 1010
- (b) 0110
- (c) 01011010
- (d) 11111110
- (e) 0011100111010011
- 2. Implement the XOR function by means of: (10%)
- (a) NAND gates only.
- (b) NOR gates only.

Please draw the gate-level circuit.

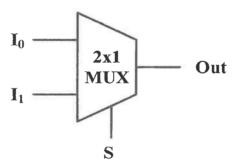- 3. Implement a 4-to-1 mux using only 2-to-1 muxes making sure to properly connect all of the terminals. Remember that you will have 4 inputs, 2 control signals, and 1 output. Write out the truth table for this circuit. (10%)
- 4. A symbol of 2-to-1 mux is listed below. Please draw the gate-level circuit of 2-to-1 mux. (10%)



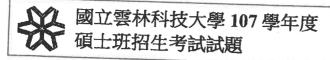- 5. Given an array of 100 elements. Write an algorithm or C program with comments to do bubble sort. Draw a flowchart. How many comparisons and how many swaps the algorithm will take at worst? What is the time complexity of this algorithm? Which sorting algorithm is faster than bubble sort? (13%)
- 6. Describe a Turing machine. What are the similarities between a Turing machine and a personal computer? What are the differences? (13%)



系所:電子系

科目:計算機概論(1)

7. Write an algorithm to find all the prime numbers less than or equal to n. Use comments to explain your program and draw a flowchart to illustrate the algorithm. Show that your algorithm work for n=25 (12%)

8. Write down the Euclidean algorithm to find the greatest common divisor between two positive integers a and b. You cannot use any division or mod function but you can use subtraction. Write down a recursive version of the Euclidean algorithm. This recursive version can use the mod function. Show that both algorithms work with two examples for each algorithm? (12%)



國立雲林科技大學 107 學年度 碩士研招生考試試題

系所:電子系

科目:電子學

本試題共五題,每題得分如各題中所示,共計 100 分,請依題號作答並將答案寫在答案 卷上,違者不予計分。

- 1. From the Voltage Transfer Characteristic (VTC), we can find four parameters of the VTC (V_{OH} , V_{OL} , V_{IL} , and V_{IH}). Determine the noise margins:
 - (a) (5 分) NMH and
 - (b) (5分) NML
- 2. For the instrumentation amplifier of Fig. P2:
 - (a) (10 分) find the voltage v_1 and v_2 .
 - (b) (10分) find the voltage v_3 and v_4 .
 - (c) (5 分) find the voltage v_0 .

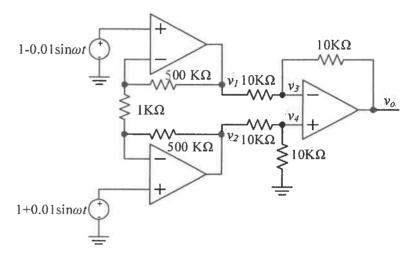


Fig. P2

- 3. Assume the forward voltage of the diode which shown in Fig. 3(a)(b)and(c) is 0.1V with no leakage current.
 - (a) (5 %) Find the values of I_l and V_l in the circuits shown in Fig. P3(a).
 - (b) (5 分) Find the values of I_2 and V_2 in the circuits shown in Fig. P3(b).
 - (c) (5 分) Find the values of I_3 and V_3 in the circuits shown in Fig. P3(c).

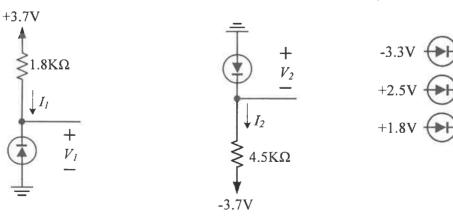


Fig. P3(a)

Fig. P3(b)

Fig. P3(c)

 $10 \text{K}\Omega$



國立雲林科技大學 107 學年度

系所:電子系

科目:電子學

4. (20分) The operational amplifiers are ideal. Please (a) calculate the voltage gains of the circuits shown in Fig. P4(a), where R1=10k Ω and R2=100 Ω . (b) Write down Vout in terms of V_A, V_B, R_A, R_B, and R_C, as shown in Fig. P4(b).

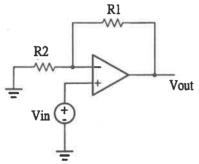


Fig. P4(a)

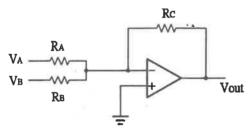


Fig. P4(b)

5. (30 分) All MOS transistors are biased in the saturation region. Neglect the body-effect of the NMOS transistors. Calculate (a) open-loop gain, (b) loop gain, and (c) closedloop gain of the feedback amplifier shown in Fig. P5. $\lambda_N = \lambda_P = 0.1 V^{-1}$. $g_{mN} = 10 \times 10^{-3} \text{ A/V}.$ $g_{mP} = 2.5 \times 10^{-3} \text{ A/V}.$ $I_{SS} = 2\text{mA}.$ $R1 = 100 \text{k}\Omega.$ $R2 = 100 \text{k}\Omega.$

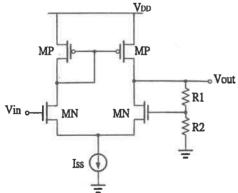


Fig. P5



國立雲林科技大學 107 學年度 碩士班招生者試試題

系所:電子系

科目:電磁學

Useful physical constants: $\varepsilon_0 \approx \frac{10^{-9}}{36\pi}$ (F/m); $\mu_0 = 4\pi \times 10^{-7}$ (H/m)

- 1. 請分別用微分與積分形式寫出基本電磁學的 4 個馬克斯威爾方程式,並解釋每個方程式的物理涵義。(12%)
- 2. 有一電位 $V = 3x^2yz$ (V) , x, y, z 代表笛卡兒座標。請寫出電場 **E** 的方程式,並計算在座標 (3 m, 2m, 1m) 處的電場。(10%)
- 3. 在原點有一個 20.0-nC 的點電荷。
 - (a) 在真空的環境下,請計算離原點 $1.0 \, \text{m}$ 處,電場 \mathbf{E} 與電通量密度 \mathbf{D} 。
 - (b) 若此電荷是埋沒在很大體積的純水環境($\epsilon_r = 81$)中,請計算離原點 1.0 m 處,電場 E 與電通量密度 D。

(使用球座標) (20%)

- 4. 有一平板電容,在結構上兩個平行電極板間的介電質是可以移除的。若此平板電容在平行電極板間沒有任何介電質時,電容值是 8 nF;填充某介電質材料後,電容值變為 32 nF。求此介電材料的介電常數(dielectric constant/relative permittivity)是多少?(8%)
- 5. 一電磁波的頻率為 108 Hz, 波長為 2 m,
 - (a) 求此電磁波的傳遞速度。
 - (b) 若此電磁波的函數為 $A_0 \cos(\omega t \beta z)$,求 ω 和 β 的值。 (20%)
- 6. 請說明:
 - (a) 磁場的單位。
 - (b) 磁通量密度的單位。
 - (c) <u>磁場和磁通量密度</u>的關係。

(12%)

- 7. 若z軸上有一無限長之導線,通有電流I(往 +z方向),
 - (a) 請說明y軸上的 (0, r, 0) 位置其磁場方向。
 - (b) 請說明 (0, r, 0) 位置其磁場大小與 r 的關係。 (18%)